

1. For the following functions, construct a truth table and draw a circuit diagram.
 1. $y(A,B) = (AB)' + B'$
 2. $y(A,B,C) = (A + B)' C$
 3. $y(A,B,C) = (AC)' + BC$
 4. $y(A,B,C) = (A \oplus B)C'$
 5. $y(A,B) = A' + B$
 6. $y(A,B,C) = ((A+B)'(B+C))'$
2. Study and verify the truth table of various logic gates
 - NOT, AND, OR, NAND, NOR, EX-OR, and EX-NOR
3. Simplify Boolean expressions and realize it.
4. Verification of Boolean Theorems using basic gates.
5. Design a 4-input NAND gate using two 2-input NAND gates and one 2-input NOR gate. Hint: Use DeMorgan's law
6. Construct the K-map for each of the following functions
 - (a) $f(A,B,C) = AB + A'BC' + AB'C$
 - (b) $g(A,B,C) = A'C + ABC + AB'$
 - (c) $h(A,B,C,D) = A'BC' + (A \oplus B)C + A'B'CD' + ABC$
7. For $g(A,B,C) = A'C + ABC + AB'$, design the circuit for the minimal SOP expression found in problem 4 using just NAND gates and inverters. Label the pinouts on the circuit diagram. Build the circuit and demonstrate the working circuit.
8. For the functions listed below, construct a K-map and determine the minimal SOP expression.
 - a. $f(a,b,c) = a'b'c' + a'bc' + abc' + abc$
 - b. $g(a,b,c) = ab'c' + abc' + abc + \text{don't cares}(a'bc + ab'c)$
 Build the circuit required for (b).
9. Design and verify a half/full adder
10. Design and verify half/full subtractor
11. Design a 4 bit magnitude comparator using combinational circuits.
12. Design and verify the operation of flip-flops using logic gates.
13. A two bit counter is to be built that will count forward, $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00$, when a logical input is set high and counts in reverse order when it is low.
 - (a) Draw the state transition diagram for this state machine.
 - (b) Assuming a state machine were to be built using D flip-flops, determine the value of the next state for each of the flip-flops.
 Build and demonstrate the state machines
14. Verify the operation of a counter.
15. Verify the operation of a 4 bit shift register

- Any open source simulator like Logisim <https://sourceforge.net/projects/circuit/> can be used.
- Breadboards/trainer kit may be used to realize logic gates

Additional resource Verilog Online simulator: www.iverilog.com/ may be used to model digital circuits and systems.